
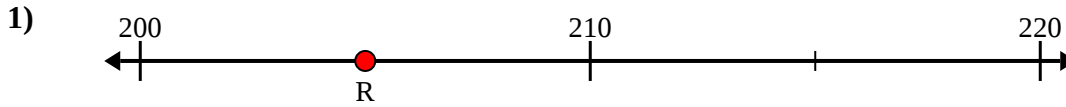


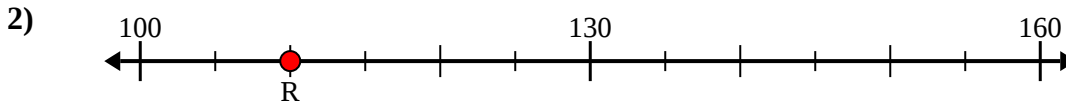


Encontrar el valor de R.

Respuestas


1. _____




2. _____

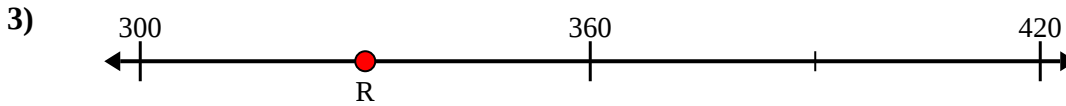


3. _____

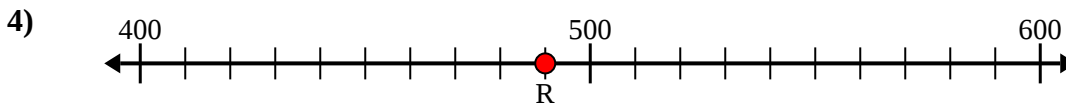


4. _____

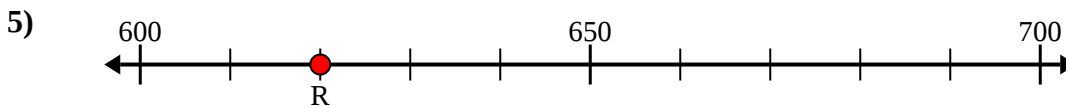


5. _____

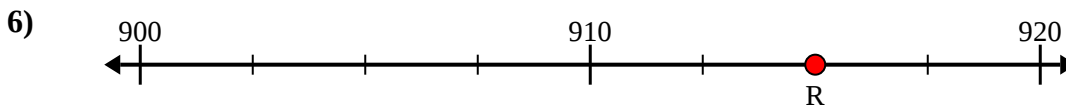


6. _____

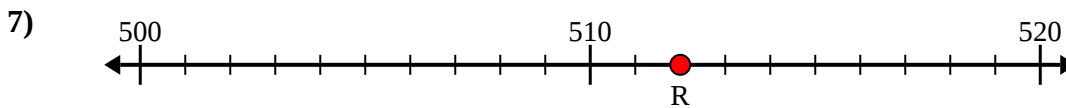


7. _____

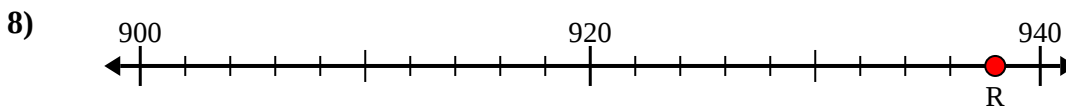

8. _____

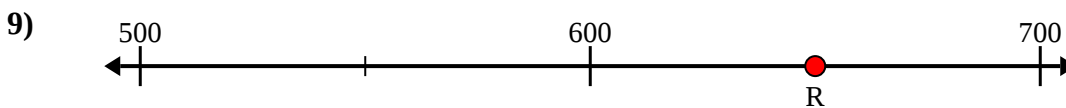







9. _____

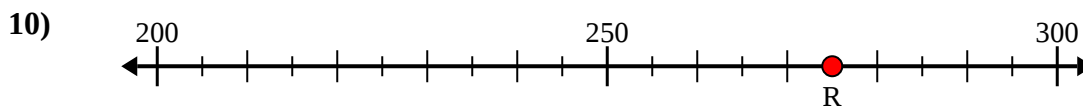

10. _____



Encontrar el valor de R.

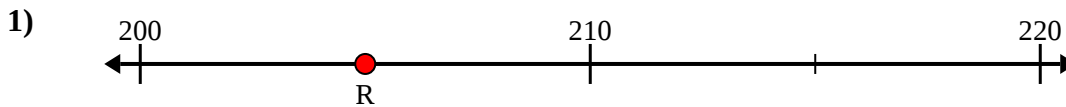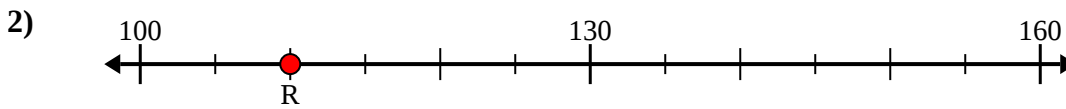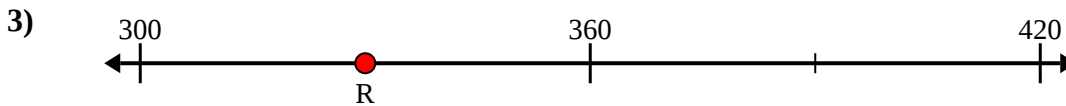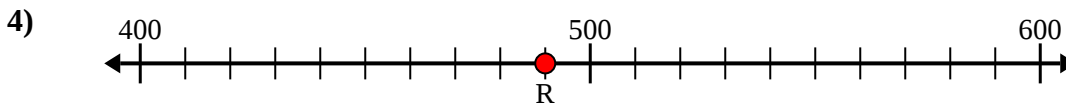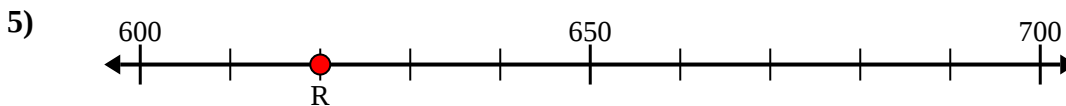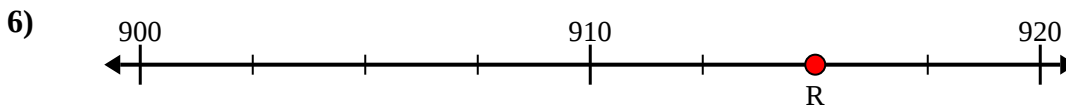Respuestas1. **205**2. **110**3. **330**4. **490**5. **620**6. **915**7. **512**8. **938**9. **650**10. **275**