
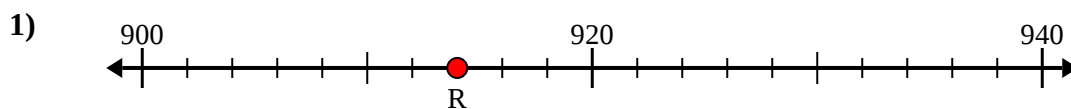


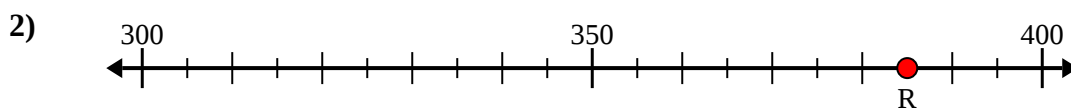


Encontrar el valor de R.

Respuestas


1. _____




2. _____

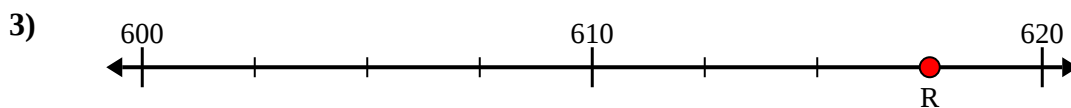


3. _____

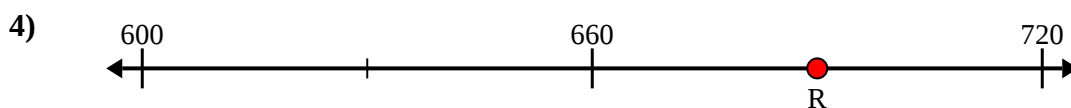


4. _____

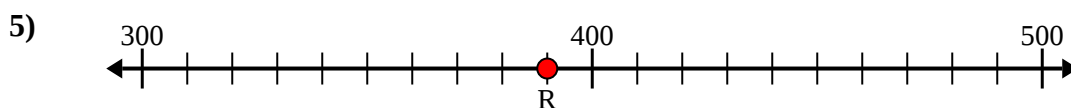


5. _____

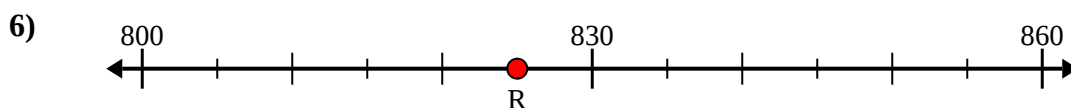


6. _____

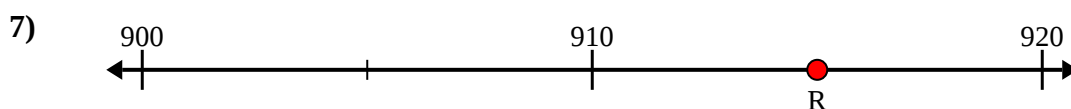


7. _____

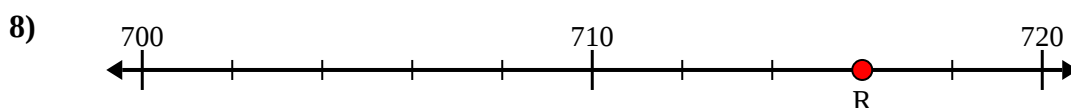

8. _____

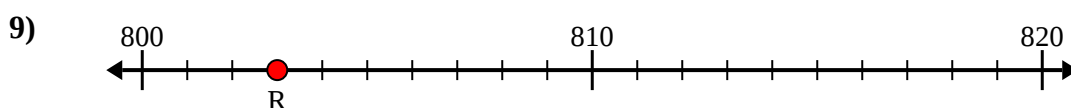











9. _____

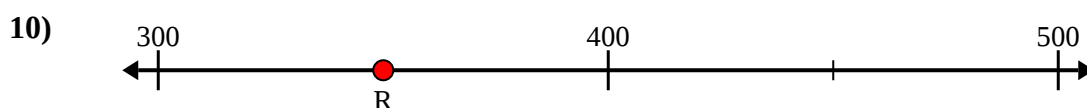

10. _____



Encontrar el valor de R.

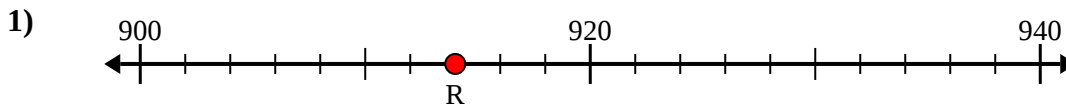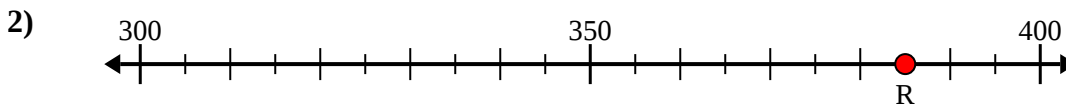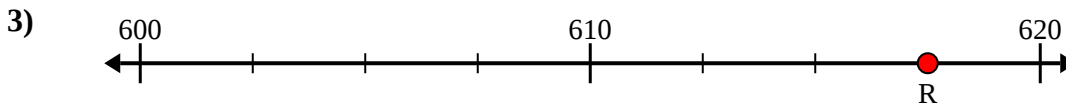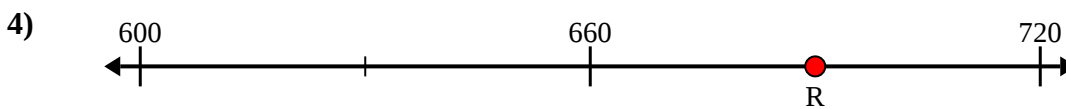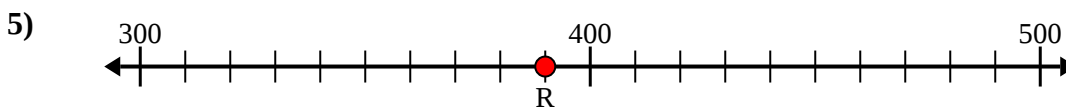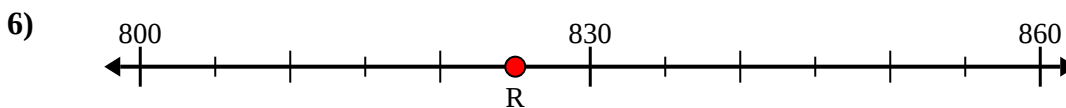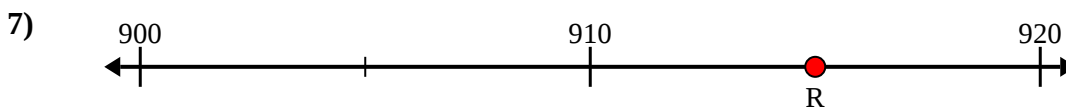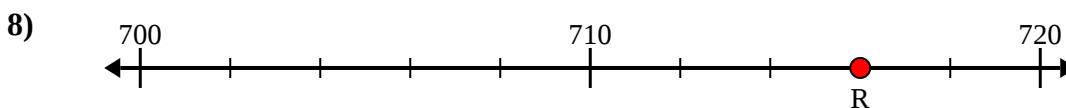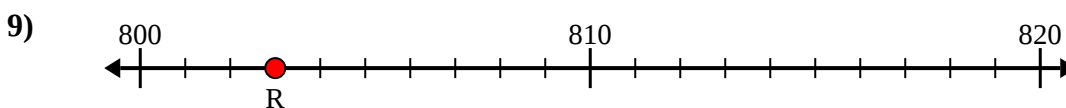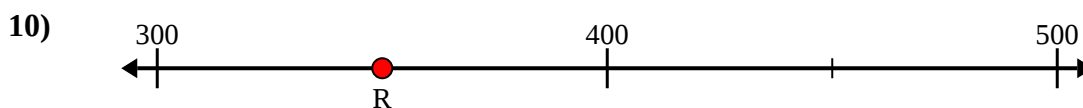Respuestas1. **914**2. **385**3. **617.5**4. **690**5. **390**6. **825**7. **915**8. **716**9. **803**10. **350**