
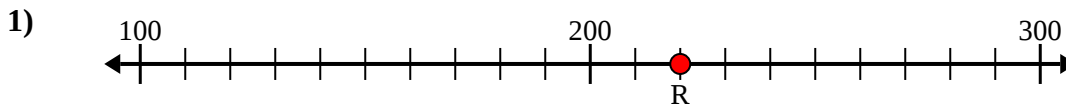


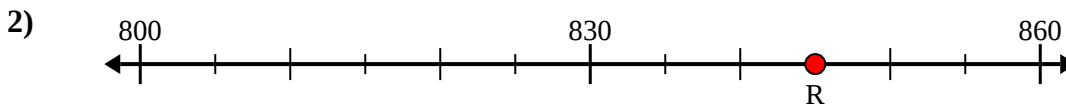


Encontrar el valor de R.

Respuestas


1. _____




2. _____

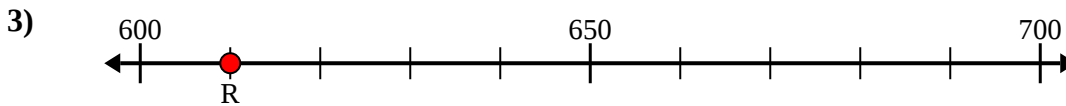


3. _____

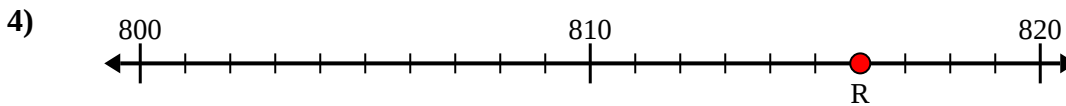


4. _____

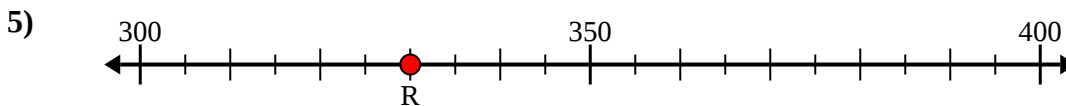


5. _____

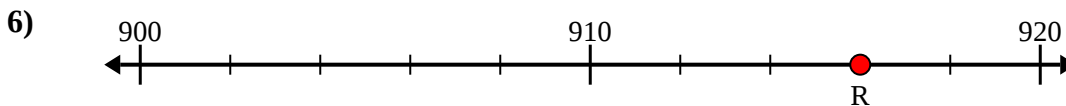


6. _____

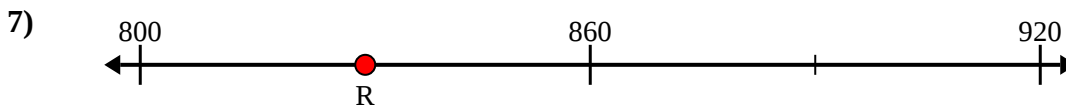


7. _____

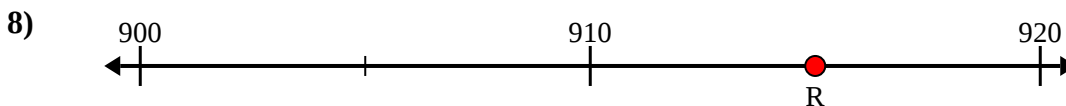

8. _____

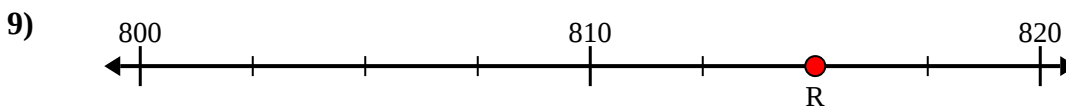











9. _____

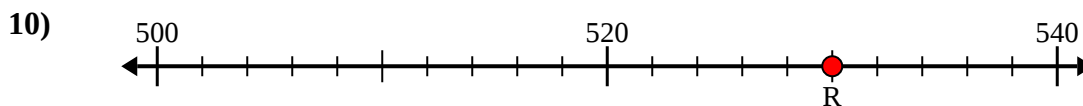

10. _____



Encontrar el valor de R.

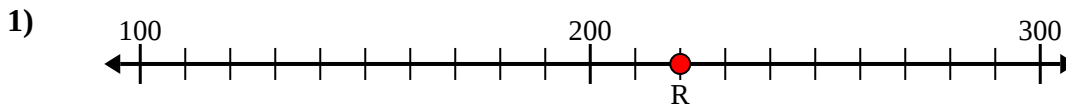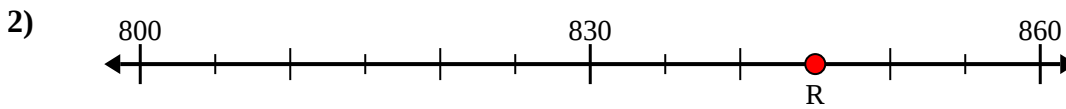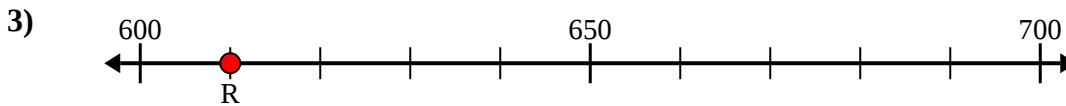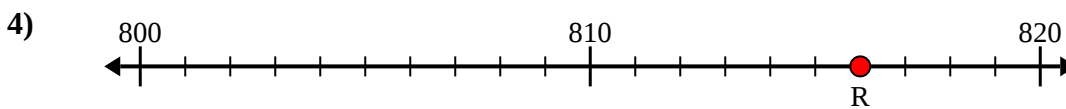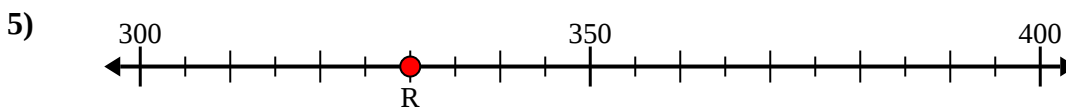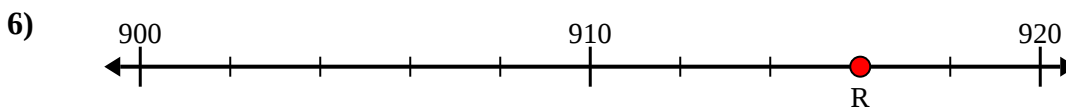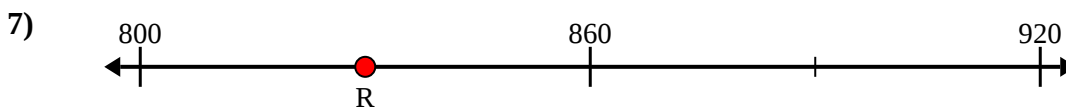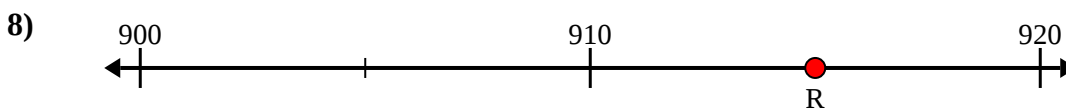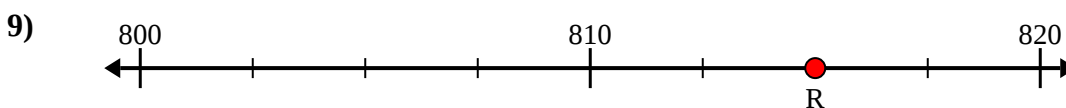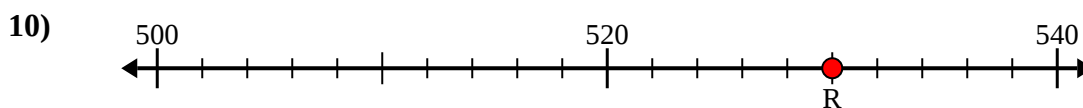Respuestas1. **220**2. **845**3. **610**4. **816**5. **330**6. **916**7. **830**8. **915**9. **815**10. **530**