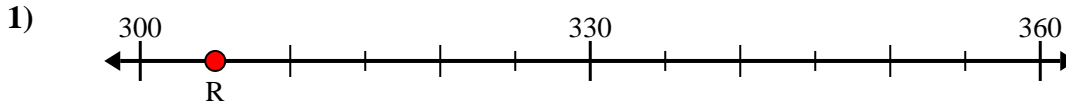





Encontrar el valor de R.


Respuestas




1. _____

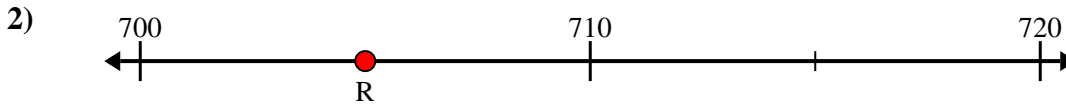


2. _____

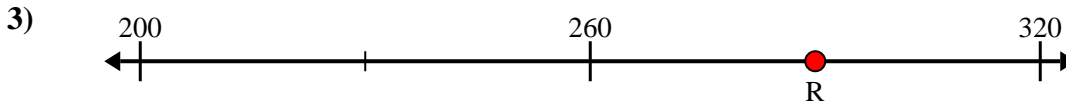


3. _____

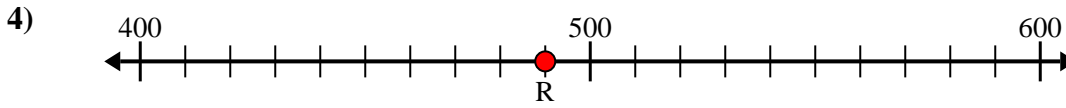


4. _____

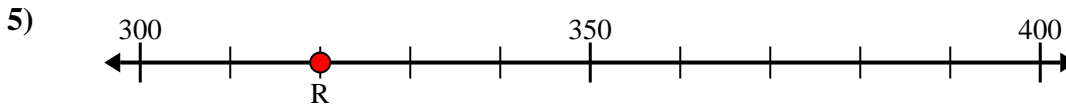


5. _____

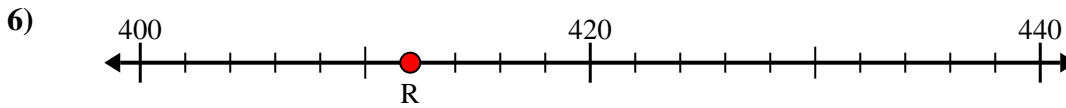


6. _____

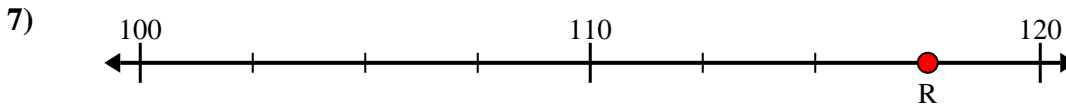


7. _____

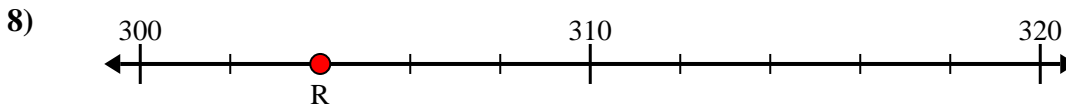

8. _____

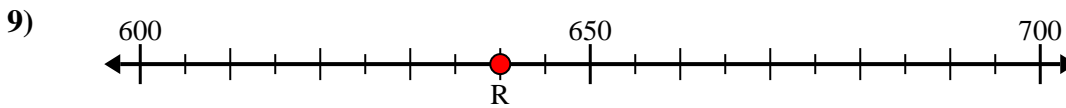

9. _____

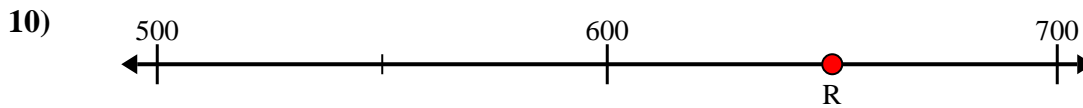


10. _____




Encontrar el valor de R.


Respuestas

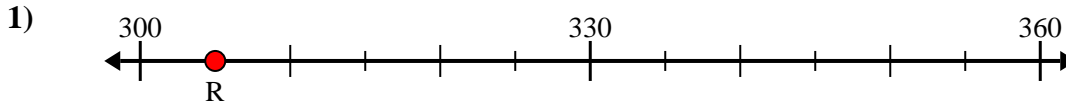

1. 305

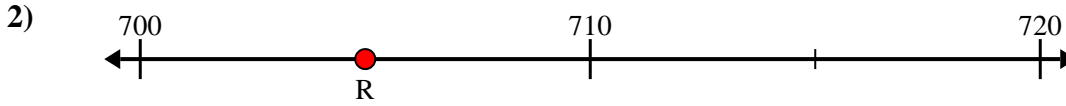


2. 705

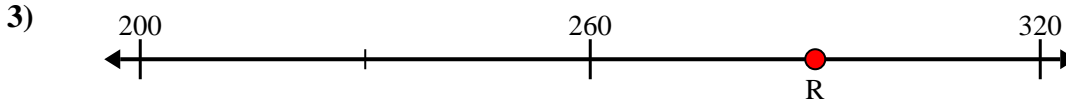

3. 290


4. 490

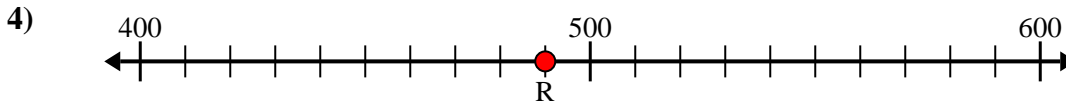

5. 320


6. 412

7. 117.5

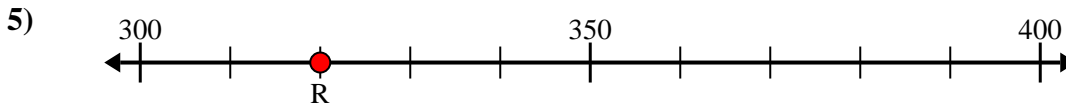

8. 304

9. 640

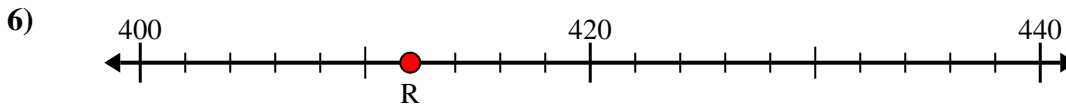

10. 650

